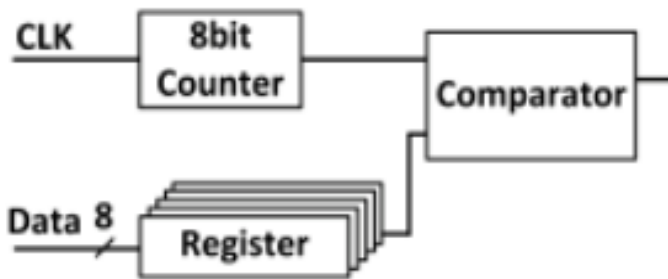


# PULSE WIDTH MODULATION GENERATOR DESIGN

A Simple PWM Signal Generator  
Design in Verilog HDL



## Introduction to PWM

- **PWM (Pulse Width Modulation):**
  - A technique used to control the power delivered to electrical devices.
  - The duty cycle (percentage of time signal is high) controls the average power.
  - Applications: Motor control, signal modulation, power supply regulation, etc.

## VERILOG CODE:

### Inputs:

- clk (Clock Signal)
- rst (Reset Signal)
- dutycycle (8-bit input for PWM duty cycle)

### Output:

- out (PWM Output Signal)

**Key Feature:** The output out generates a square wave with a duty cycle controlled by the dutycycle input.

### Registers:

- counter: An 8-bit register that counts clock cycles.

## Behavior:

- The counter increments on every clock cycle.
- The PWM output is high when the counter is less than the duty cycle.

## Always Block:

- Triggered by positive edge of `clk` or `rst`.
- If `rst` is active, reset counter to 0 and output `out` to 0.
- If `rst` is not active, increment the counter and check if the counter value is less than the `dutycycle`.

## PWM Generation Logic:

- If the counter value is less than the `dutycycle`, set `out` to high (1).
- Otherwise, set `out` to low (0)


# Working of the PWM Generator

## Clock Driven:

- The clock signal (`clk`) drives the timing of the PWM signal.

 
## Duty Cycle Control:

- The dutycycle input adjusts the high time of the PWM signal.
- A dutycycle of 128 (50%) means the PWM signal is high for half the time and low for the other half.


 
## Applications of PWM

- **Motor Control:**
  - Varying the duty cycle can control the speed of DC motors.
- **Signal Modulation:**
  - Used in communication systems and signal encoding.
- **Power Control:**
  - Efficient power delivery in power electronics.



## Conclusion:

The PWM generator in Verilog is a simple yet powerful way to control the pulse width modulation signal based on an input duty cycle.